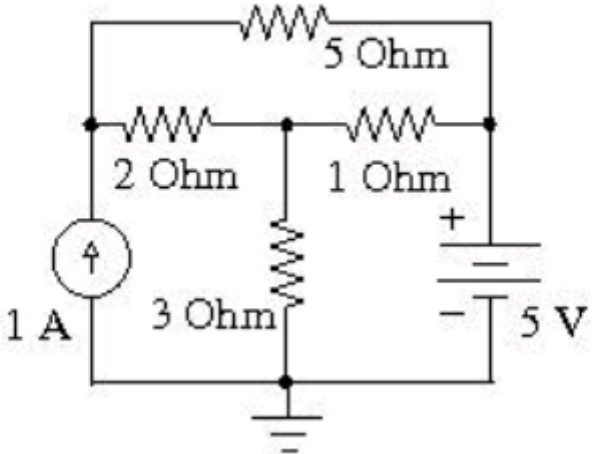
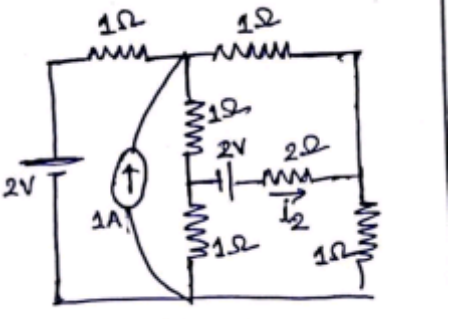
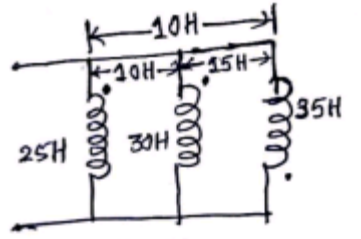
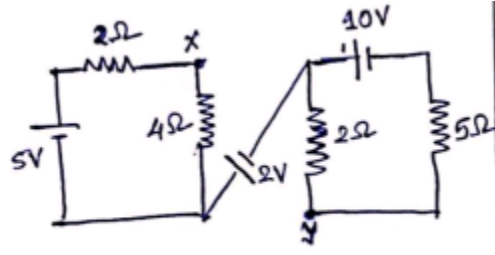
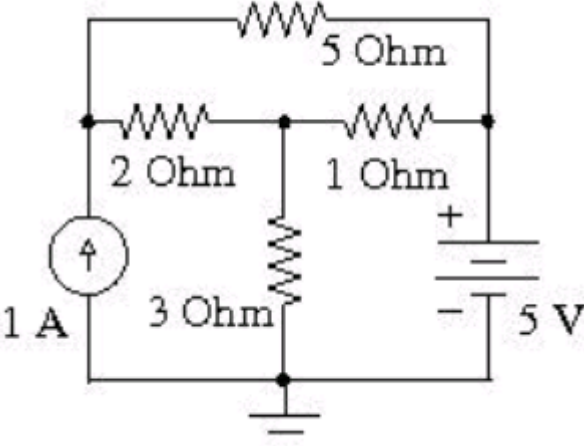
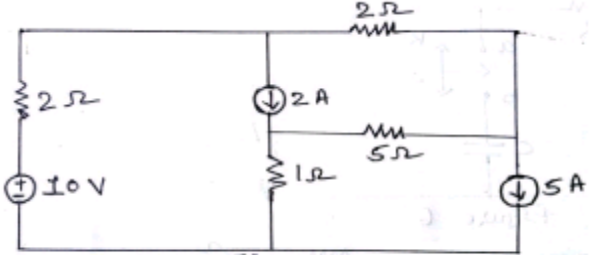
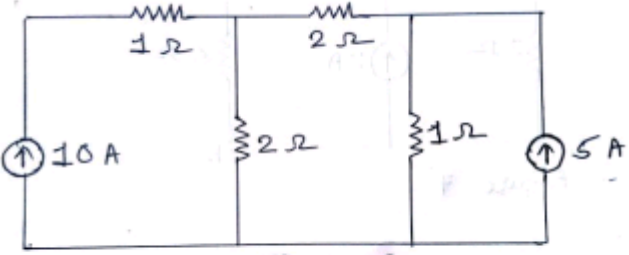
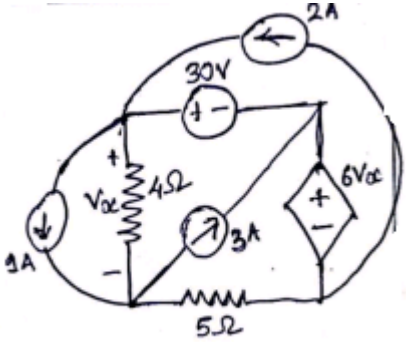
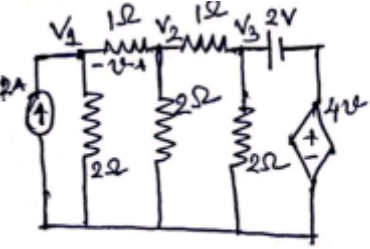


1	CIRCUIT VARIABLES AND CIRCUIT ELEMENTS AND SOURCES				
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	Mention the relations between voltage and current for the following passive elements. (1) Resistor (2) Capacitor.	3			
2.	Draw the characteristics and differentiate between ideal current source and actual current source.	4			
3.	<p>Find the current passing through the 2 Ohm resistor using Mesh analysis for the circuit shown in the following figure.</p> 	7			
4.	Explain the characteristic of an ideal current source.		3		
5.	Write the voltage current relationships of pure inductor and pure capacitor.		4		
6.	Explain characteristic of an ideal current source.			4	



7.	Define following terms: (a) Linear and Nonlinear Networks (b) Lumped and Distributed Networks				3
8.	<p>In the network of figure:2 , determine the i_2 using Source Transformation method.</p>  <p>Figure:2</p>				7
9.	<p>Determine the inductance between the terminals for a 3 coil shown in figure:3.</p>  <p>Figure:3</p>				3
10.	<p>Find the voltage drop across x-y for figure:4</p>  <p>Figure:4</p>				4

2	NODAL ANALYSIS AND MESH ANALYSIS OF RESISTIVE CIRCUITS				
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	Explain the principle of source transformation to obtain equivalent voltage source from a current source.	3			
2.	Briefly describe the nodal analysis with a small example.	4			
3.	<p>Find the current passing through 3 Ohm resistor in the following circuit using nodal analysis.</p> 	7			
4.	Briefly explain the mesh analysis.		3		



5.	Differentiate between mesh analysis and nodal analysis		4		
6.	Explain principle of source transformation to obtain equivalent current source from a voltage source.			3	
7.	<p>Find the value of all currents and voltage across 5Ω resistor for the network shown in figure 2 using mesh analysis.</p>  <p style="text-align: center;">Figure 2</p>			7	
8.	<p>Apply nodal analysis for the network shown in figure 3 and find current across 2Ω resistor connected between two nodes.</p>  <p style="text-align: center;">Figure 3</p>			7	
9.	Find the value of V_x in the circuit of figure:5, using mesh analysis.\				7


	 <p>Figure: 5</p>				
<p>10.</p>	<p>In the network of figure:6, determine the node voltages V_1, V_2, V_3 using node analysis.</p>  <p>Figure: 6</p>				<p>7</p>


3	CIRCUIT THEOREMS AND THEIR APPLICATION IN ELECTRIC NETWORKS				
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	<p>Obtain the value of Norton's equivalent current and Norton's equivalent resistance for the network shown in the following figure.</p> <div style="text-align: center;"> <p>Values of all resistors are in Ohms</p> </div>	7			
2.	Briefly describe Millman's theorem.	3			
3.	Obtain the value of Thevenin's equivalent voltage and Thevenin's equivalent resistance for the network shown in the following figure.		7		

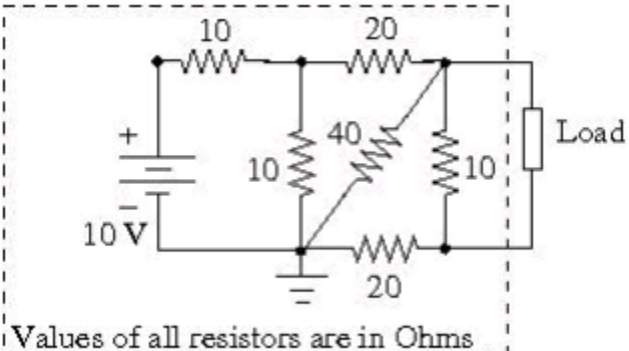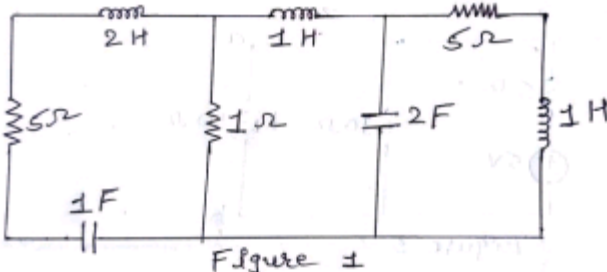	 <p>Values of all resistors are in Ohms</p>				
4.	Briefly describe superposition theorem.		3		
5.	Explain the reciprocity theorem.		4		
6.	<p>Draw the dual of network shown in figure</p>  <p>Figure 1</p>			4	
7.	State and explain maximum power transfer theorem.			3	
8.	Find voltage V_X in the network shown in figure 4 using superposition theorem.			7	


	<p>Figure 4</p>				
9.	State and explain Millman's theorem.			3	
10.	Find Thevenin's equivalent circuit for the network shown in figure 5. Also find power dissipated in R_L .	<p>Figure 5</p>			7
11.	State and explain Superposition theorem.			3	
12.	Find Norton's equivalent circuit for the network shown in figure 7. Obtain current through 5Ω resistor.	<p>Figure 7</p>			7


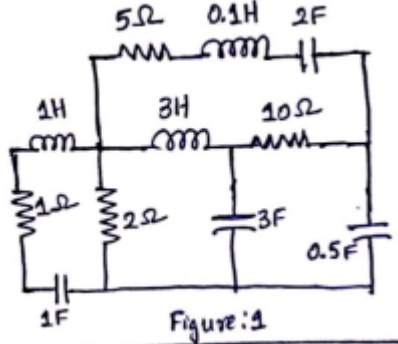
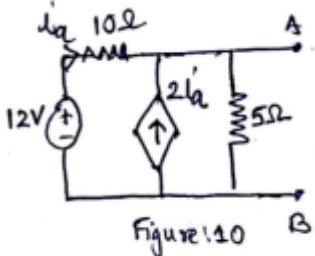
13.	<p>Construct the exact dual of the network of figure:1.</p>  <p>Figure:1</p>				4
14.	State and explain superposition's theorem.				3
15.	State and explain Maximum Power Theorem.				3
16.	<p>Find the Norton's equivalent circuit across terminals AB of the circuit shown in figure:10.</p>  <p>Figure:10</p>				7
17.	Find the Thevenin's equivalent network across the terminals A and B for figure:11.				7


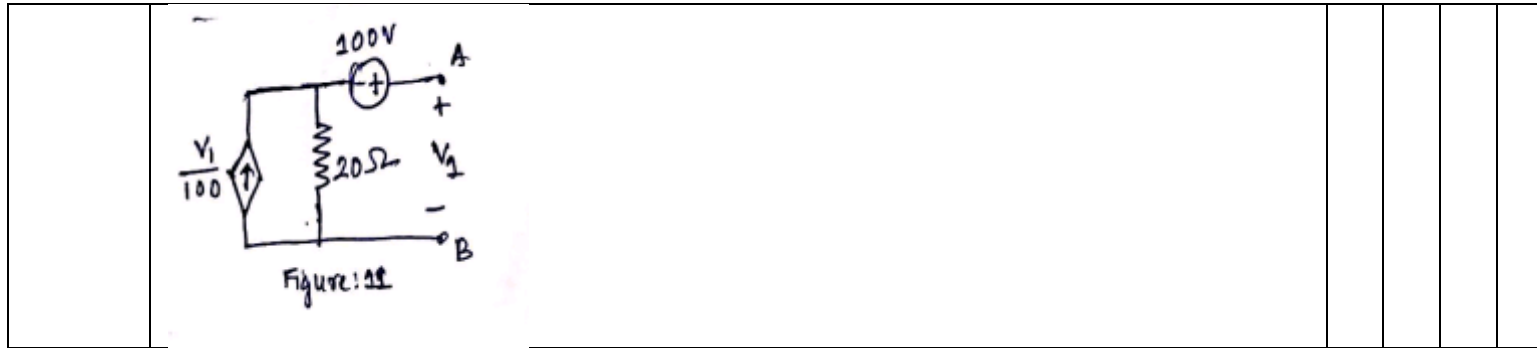


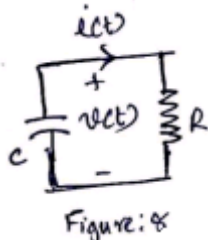4	TIME DOMAIN RESPONSE OF FIRST ORDER RL AND RC CIRCUITS				
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	Derive the equation of inductor current and draw its waveform for a series R-L circuit connected to a step input voltage.	4			
2.	What do you mean by a first order system? Give two examples of first order systems. Explain the procedure to obtain the transient response of a first order system.	7			
3.	Explain the time response of R-L-C series circuit with step input. Assume critically damped system.		4		
4.	How the following elements will behave at $t = 0$ and $t = \infty$. Draw the equivalent network as well. (a) Inductor (b) Capacitor.				4
5.	In the circuit shown in figure:8, voltage and current expressions are $v(t) = 100e^{-1000t}V, t \geq 0$ and $i(t) = 5e^{-1000t}mA, t \geq 0$. Find (a) R, C and Time Constant (τ). (b) Initial energy stored in capacitor. 				4
6.	Explain and derive the step response to R-L series circuit using Laplace Transformation method				4


5		TIME DOMAIN RESPONSE OF SECOND ORDER LINEAR CIRCUITS			
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	With suitable example explain how the Laplace transform is useful in obtaining the transient response of a second order system.	7			
2.	Take suitable example of a first order system and explain the procedure to obtain its transient response.		7		
3.	What is time constant? What is its significance?				3


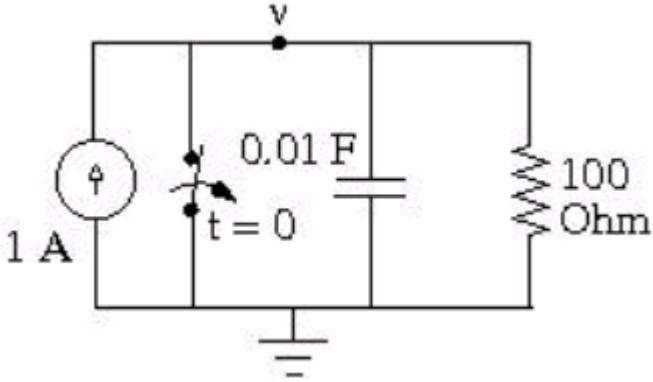
6	INITIAL CONDITIONS				
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	<p>Find out the values of 'v' ; 'dv/dt' and '$d^2 v/dt^2$' just after switching (at time $t = 0+$) in the circuit shown in the following figure.</p> 	7			
2.	Describe the steps to evaluate the initial conditions of a network.	3			
3.	Find out the values of ' i ' ; ' di/dt ' and ' $d^2 i/dt^2$ ' just after switching (at time $t = 0+$) in the circuit shown in the following figure.		7		

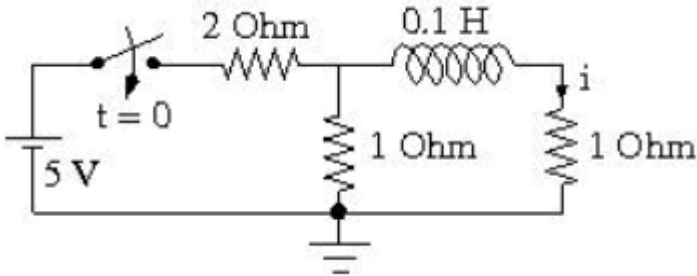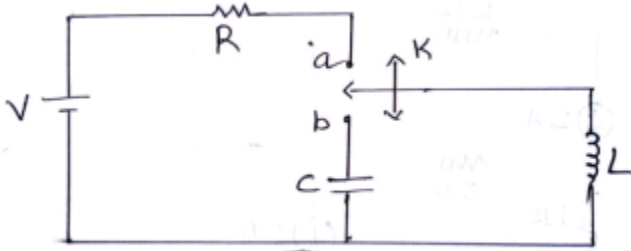
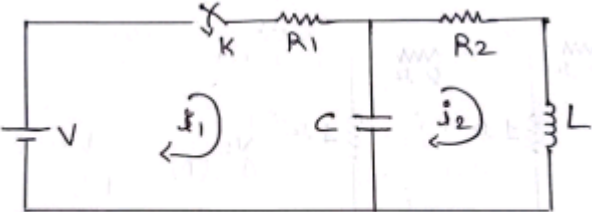
					
4.	Briefly describe the rules for initial conditions calculation of various circuit elements.		7		
5.	<p>In the network shown in figure 6, switch k is moved from position a to position b at $t=0$. Find current $i(t)$ using Laplace transformation method.</p>  <p style="text-align: center;">Figure 6</p>			4	
6.	State and explain initial value theorem.			3	
7.	<p>In the network shown in figure 8, find i_1, i_2, di_1/dt and di_2/dt at $t=0^+$ assuming all initial conditions as zero.</p>  <p style="text-align: center;">Figure 8</p>			4	


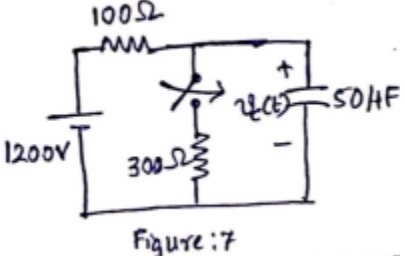
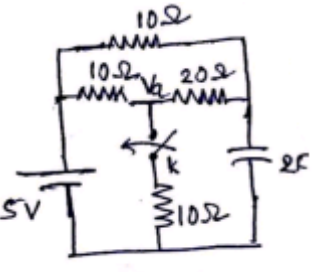
8.	<p>A series RLC circuit having with zero inductor current and zero capacitor voltage is excited by 20 V dc source. Find $i(0^+)$ and $di/dt(0^+)$. Take $R=10\Omega$, $C=10\mu\text{F}$, $L=2\text{H}$. (A switch K is also connected in series with RLC.)</p>			7	
9.	<p>For the network shown in figure:7, the switch k is open for a long time and closed at $t = 0$. Determine $v_c(t)$.</p>  <p style="text-align: center;">Figure:7</p>			7	
10.	<p>In a network of figure:9, a steady state is reached with the switch k open. At $t=0$, the switch is closed. Determine the values of $v_a(0^-)$ and $v_a(0^+)$.</p>  <p style="text-align: center;">Figure:9</p>			7	


7	LAPLACE TRANSFORM ANALYSIS AND CIRCUIT APPLICATIONS				
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	<p>(a) Find out the poles of the system described in the immediately next question i.e. Q-3(b). 03</p> <p>(b) Write the circuit equations for a series RC circuit connected to a DC supply. Using Laplace transform, obtain the transfer function between capacitor voltage and supply voltage. 04</p>	7			
2.	Write the circuit equations for a series RL circuit connected to a DC supply. Using Laplace transform, obtain the transfer function between Inductor current and supply voltage.		3		
3.	Find the poles of the system described in previous question i.e. Q-2 (above question mentioned)		4		
4.	Briefly describe the application of Laplace transform for transfer function approach in circuit analysis.		7		
5.	What is impulse function? Find the impulse response for the network function $H(S)=5/(S^2+S+1)$			4	
6.	Derive Laplace Transform of $f(t) = tu(t)$.				3
7.	State the procedure to obtain solution of a network using Laplace Transform method. State advantages of Laplace method over classical method.				4

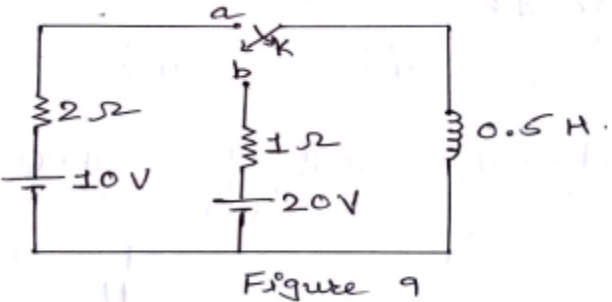8	LAPLACE TRANSFORM ANALYSIS AND TRANSFER FUNCTION APPLICATIONS				
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	Explain the procedure to obtain sinusoidal steady state response of a circuit.	7			
2.	<p>In the network shown in figure 9, switch K is moved from a to b at $t=0$, steady state having previously been attained. Determine current $i(t)$.</p>  <p style="text-align: center;">Figure 9</p>			7	
3.	Using Laplace transformation, solve the following differential equation. $d^2 i / dt^2 + 4 di / dt + 8i = 8u(t)$. Given that $i(0^+) = 3$ and $di / dt (0^+) = -4$.				4

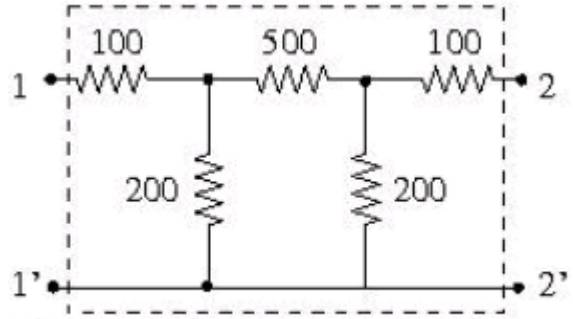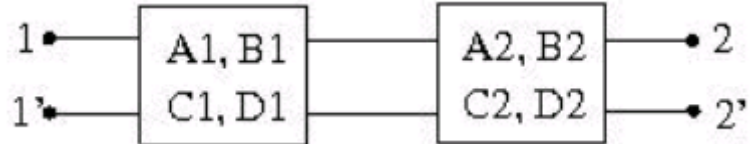9	TWO PORT NETWORKS				
Sr. No.	Questions	Dec - 15	NOV - 16	NOV - 17	MAY - 18
1.	<p>Find out the Z-parameters of the two port network shown in the following figure.</p>  <p style="text-align: center;">Values of all resistors are in Ohms</p>	7			
2.	<p>Find out the equivalent ABCD parameters of the cascade combination of two networks as shown in the following figure.</p> 	3			
3.	<p>Find out the Y-parameters of the network shown in the following figure.</p>	4			

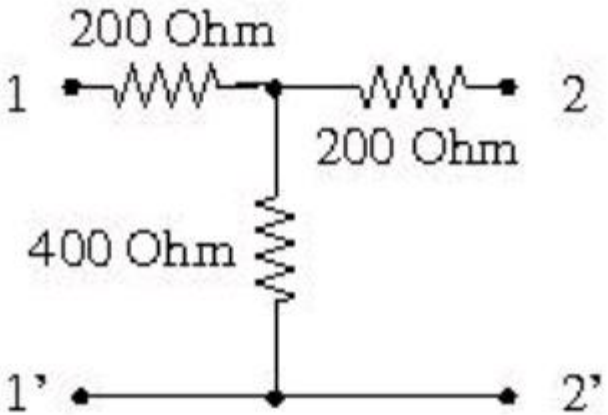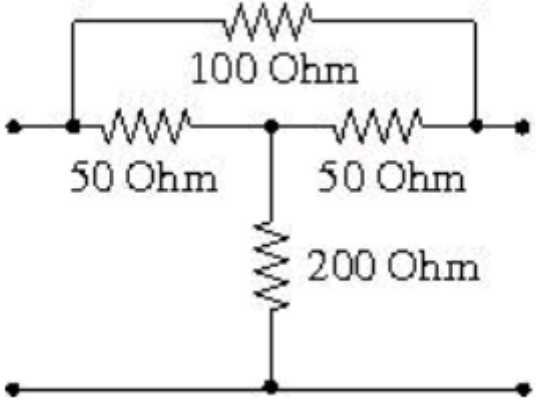					
4.	<p>Find out the Z-parameters of the two port network shown in the following figure.</p> 		7		
5.	<p>Briefly describe ABCD parameters and inverse ABCD parameters for a symmetric two port network.</p>		3		
6.	<p>Find out the Y-parameters of the network shown in the following figure.</p>		4		

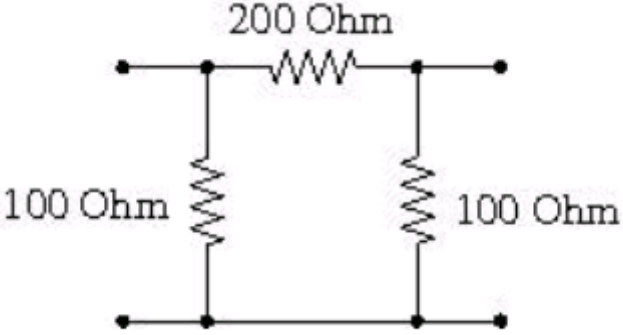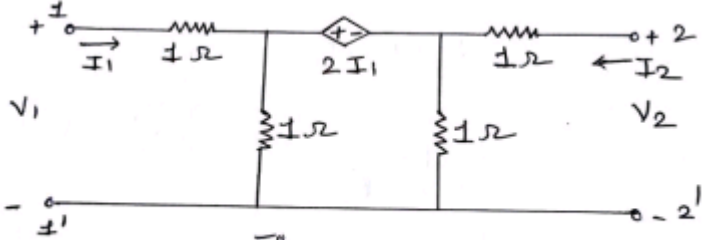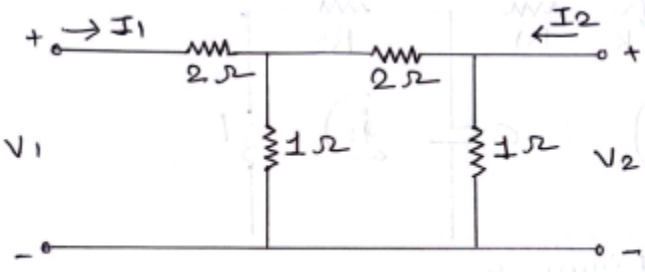					
7.	Give relationship between y parameters and h parameters.			4	
8.	<p>Find Z-parameters for the network shown in figure 11.</p>  <p>Figure 11</p>			7	
9.	<p>Obtain ABCD parameters for the network shown in figure 12.</p>  <p>Figure 12</p>			7	

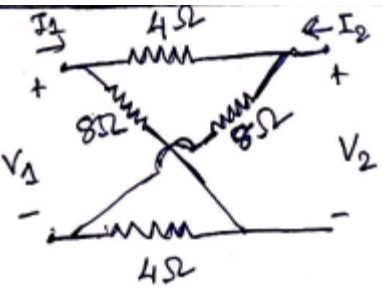10.	Write equations of Short circuit Admittance and Open Circuit Impedance parameters of a two port network.				3
11.	Derive formulae to convert given y – parameters into h - parameters.				4
12.	<p>For the network of figure: 12, find the z and y parameters.</p>  <p>Figure: 12</p>				7