

ASSIGNMENT: 5 SEQUENTIAL CIRCUIT AND SYSTEM

1. How to generate 8x1 MUX using 4x1 MUX.
2. Implement the following Boolean functions with a multiplexer and Decoder. $F(w, x, y, z) = \Sigma (2, 3, 5, 6, 11, 14, 15)$
3. Design a combinational logic circuit whose output is high only when majority of inputs (A,B,C,D) ARE LOW
4. Implement the following function with NAND and NOR Gate. $F(a,b,c) = \Sigma (0,6)$
5. Simplify the following Boolean functions to a minimum numbers of literals.
1. $x + x'y$ 2. $x(x'+y)$ 3. $x'y'z + x'yz + xy'$ 4. $xy + x'z + yz$