

Assignment: 1

1. Explain V-I Characteristic of SCR.
2. Explain Two Transistor Analogy of SCR.
3. What are the different methods for turning off an SCR? Explain class C Commutation with its necessary circuit and waveform
4. Define 1. Latching current 2. Holding current
5. Explain the triggering mode of TRIAC with its structure diagram and characteristic

