

Assignment: 2

1. Draw necessary waveforms and explain working of 1- ϕ full controlled rectifier circuit with R-L load.
2. Explain working of 1- ϕ semi converter with resistive load..
3. Describe the uses of freewheeling diode in converters circuit.
4. Explain the concept of 'Dual Converter'. Using circuit diagram, briefly explain the working of anyone type of dual converter.
5. Explain working of single phase half converter with R load.

