

### Assignment: 3

1. Explain the various performance parameter used for inverter
2. Explain the working of 1 phase full bridge inverter with help of circuit diagram and waveforms.
3. Explain the operation of a PWM inverter.
4. Explain three phase inverter with 180 mode of conduction.
5. Explain forced commutation and line commutation.

